

Introduction

This is a group assignment on using digital *logic gates* and design more complex digital *circuits*.

Assignment Goals

Learning Outcomes After completing this group assignment, each student is expected to be able to

- **Draw** truth tables for a given logic circuit or expression.
- **Draw** a logic circuit for a given truth table.
- **Create** different “simple” gates from other “simple” gates.

Procedure

Get out paper for a *single* turn-in at the end of class. Copy enough of each question so that the paper could stand alone as a study guide.

Assign (Least-recently Held) Roles: *Manager, Recorder, Reflector, Speaker*. Everyone should help the whole team contribute and manage time.

Answer these questions:


1. Draw the *truth-table* for each of the circuits below.




2. Using just the gate below, construct circuits that are logically equivalent to **AND**, **OR**, and **NOT** (you may want to do them in a different order).



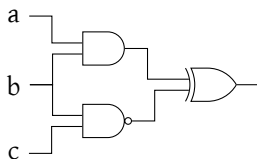3. Using only two-input **AND** gates, construct a *three-input AND* gate. Before starting, make sure you understand the desired truth-table (no need to draw it).
4. Draw the truth table for the following circuit:



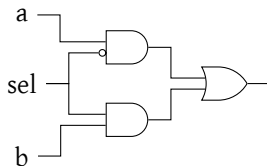5. Draw the truth table for the following circuit. Put the *sel* column on the left of the table.



6. Add the *binary* numbers 0101 and 0111; interpreting them (and their sum) as *unsigned* values, what sum did you just calculate, in decimal?
7. Consider a **full-adder** that could add the two numbers from above. How many *carry-in* wires would you need? How many *carry-out*? How many wires of input and how many for output?
8. Draw a *three-input* circuit that determines if exactly two of its inputs are 1. You may only use two-input **AND**, **OR**, and **NOT** gates.