

Introduction

This assignment is a *group* assignment. If I, in the room, do not **hear** you interacting with the other students, you are doing it *wrong!*

Assignment Goals

Learning Outcomes After completing this group assignment, each student is expected to be able to

- *Implement* a PC with a Register and combinatorial logic.
- *Discuss* simpler PC variants (and see their implementation).

Procedure

Get out paper for a *single* turn-in at the end of class. Copy enough of each question so that the paper could stand alone as a study guide.

Assign Roles. Manager, Recorder, Reflector, Speaker.

Answer these questions.

1. What is the difference between *combinatorial* circuits and *synchronous* circuits? Answer in terms of when **outputs** change relative to when **inputs** change.
2. Given an unlimited number of sequential circuits (including plexers and adders) and one (1) 32-bit Register, construct a SimpleProgramCounter that has a 32-bit output (its current value) and increments by 4 on every clock tick.
3. What makes the SimpleProgramCounter less useful than a proper ProgramCounter? What *can't* it do?
4. Modify the SimpleProgramCounter to a PausableSimpleProgramCounter: it has an input, run, and it increments only on clock ticks while run is high.
5. Extend the **SimpleProgramCounter** to a LoadableSimpleProgramCounter: it has inputs: D with a new value to load; en to *enable* loading the new value. On a clock tick, if en, latch D, otherwise latch Q plus 4.
6. Extend the LoadableSimpleProgramCounter to a ProgramCounter. Inputs are extended with a reset flag: if reset, latch 0.

reset	en	Latch
0	0	Q+4
0	1	D
1	0	0
1	1	0

7. Which flag, en or reset, has *priority* in the ProgramCounter circuit?
(No need to write the whole circuit.) How would you reverse the priority between them?